

BLM/COM275**2021-2022 Fall****Homework-3****Due Date:** 6.12.2021 11:59 p.m.

Answer on paper and upload the photo of the solutions to the system in pdf format. The name of the file you uploaded to the system should be "**StudentNumber.pdf**". Also, bring your answer paper with you at your lab time and hand it in.

Q1. Simplify the following Boolean functions, using Karnaugh maps:

a) $F(w, x, y, z) = \sum(1, 4, 5, 6, 7, 13)$

b) $F(w, x, y, r) = \sum(0, 1, 5, 8, 9)$

Q2. Find the minterms of the following Boolean expressions by first plotting each function in a map:

a) $wyz + w'x' + wxz'$

b) $A'B + A'CD + B'CD + BC'D'$

Q3. Simplify the following Boolean functions to product-of-sums form:

a) $F(w, x, y, z) = \sum(0, 1, 2, 5, 8, 10, 13)$

b) $F(A, B, C, D) = \prod(1, 3, 6, 9, 11, 12, 14)$

Q4. Simplify the following functions, and implement them with two-level NAND gate circuits:

a) $F(A, B, C, D) = A'B'C + AC' + ACD + ACD' + A'B'D'$

b) $F(A, B, C) = (A' + B' + C')(A' + B')(A' + C')$

Q5. Draw a logic diagram using only two-input NOR gates to implement the following function:

$$F(A, B, C, D) = (A \oplus B)'(C \oplus D)$$

Q6. Implement the following Boolean function F , together with the don't-care conditions d , using no more than two NOR gates :

$$F(A, B, C, D) = \sum(2, 4, 6, 10, 12)$$

$$d(A, B, C, D) = \sum(0, 8, 9, 13)$$

Q7. Implement the following Boolean function F , using the two-level forms of logic (a) NAND-AND, (b) AND-OR, (c) OR-NAND, (d) NOR-OR:

$$F(A, B, C, D) = \sum(0, 4, 8, 9, 10, 11, 12, 14)$$

Q8. Implement the following Boolean expressions with three half adders:

a) $D = A \oplus B \oplus C$

b) $F = ABC' + (A' + B')C$